

四、功率为 40 W、功率因数为 0.5 的日光灯(为感性负载)与功率为 60 W 的白炽灯(为纯阻性负载)各 100 只, 并联接于 220 V、50 Hz 的正弦交流电源上。

(1) 求电路的功率因数;

(2) 如果把电路的功率因数提高到 0.9, 则应并联多大的电容?

解(1)

$$P_{\Sigma} = 100 \times 40 \times 0.5 + 100 \times 60 \times 1$$

~~$100 \times 40 + 100 \times 60$~~ 总的视在功率不是各支路视在功率的代数和, 视在功率不能直接相加

$$= \frac{8000}{10000} = 0.8$$

解(2)

$$P_{\Sigma i} = 40 \text{ W} \quad (i=1, 2, \dots, 100), \quad Q_{\Sigma i} = 40\sqrt{3} \text{ W} \quad (i=1, 2, \dots), \quad \tilde{S}_{\Sigma i} = 40 + 40\sqrt{3}j \text{ VA}$$

$$P_{\Sigma i} = 60 \text{ W} \quad (i=1, 2, \dots, 100), \quad Q_{\Sigma i} = 0 \text{ W} \quad (i=1, 2, \dots), \quad \tilde{S}_{\Sigma i} = 60 \text{ VA}$$

$$\cancel{\tilde{Q}_{\Sigma} = \sum_{i=1}^{100} (0)}$$

$$\tilde{S}_{\Sigma} = \sum_{i=1}^{100} (\tilde{S}_{\Sigma i} + \tilde{S}_{\Sigma i}) = 4000 + 4000\sqrt{3}j + 6000 = 10000 + 4000\sqrt{3}j \text{ VA}$$

$$\cos \theta_{\Sigma} = \frac{10000}{10000} \quad \frac{P_{\Sigma}}{|\tilde{S}_{\Sigma}|} = \frac{10000}{\sqrt{10000^2 + (4000\sqrt{3})^2}} = 0.822$$

(2)

对电容支路

$$\dot{I}_C = \frac{\dot{U}}{-j\frac{1}{\omega C}} = \frac{220 \angle 0^\circ}{-j\frac{1}{100\pi C}}$$

$$\therefore \dot{I}_C = 22000C \cdot \pi \angle 90^\circ$$

$$\therefore \cos \theta_C = -90^\circ$$

$$\therefore \tilde{S}_C = \frac{U \dot{I}_C}{\sqrt{2}} \sin(-90^\circ) = -4840000C\pi j$$

$$\therefore \cos \theta_{\Sigma'} = \frac{P_{\Sigma}}{|\tilde{S}_{\Sigma'}|} = \frac{10000}{\sqrt{(10000)^2 + (4000\sqrt{3} - 4840000C\pi)^2}} = 0.9 \quad \therefore C = 1.37 \times 10^{-4} \text{ F}$$

