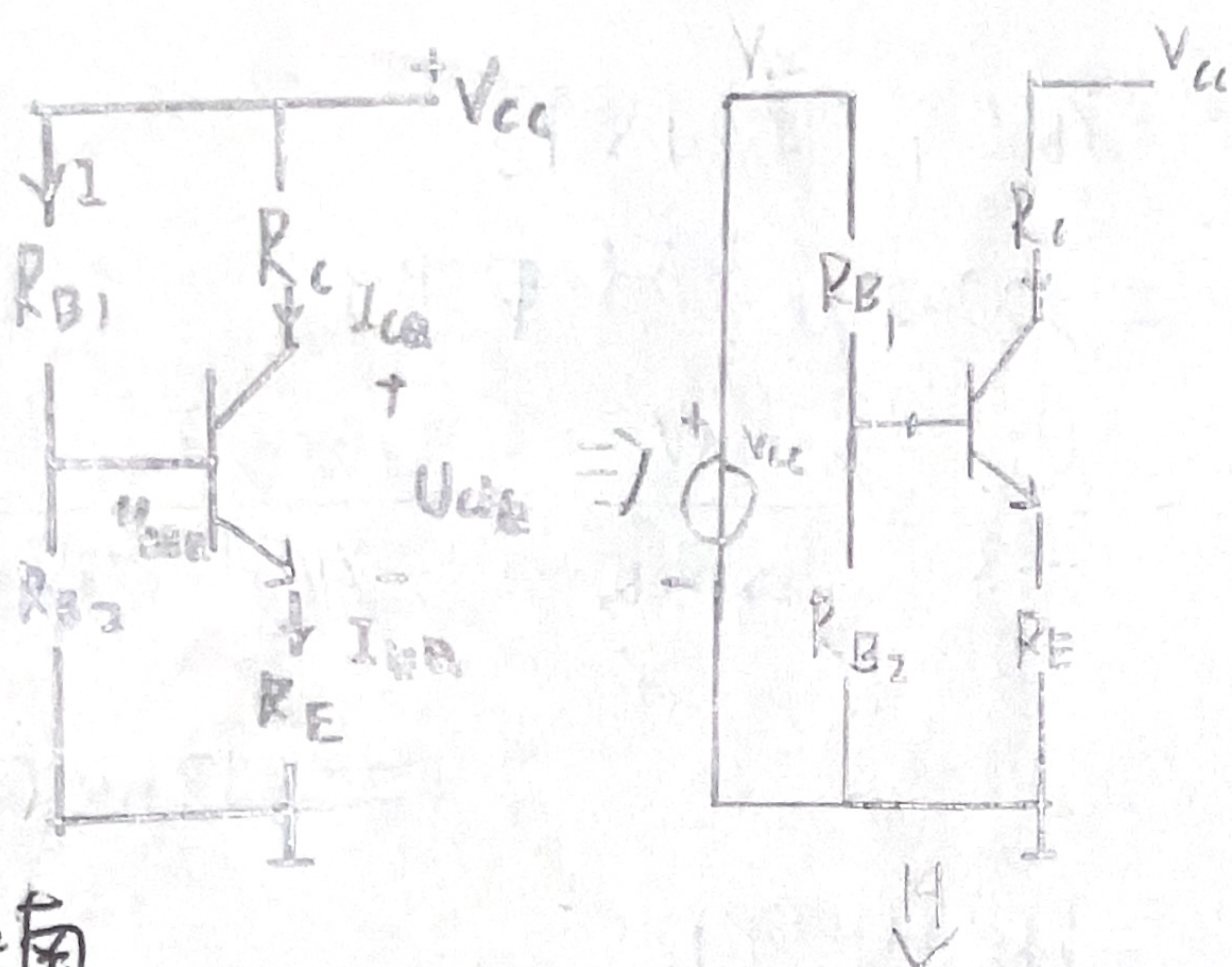


二、

共射

直流通路:



戴维南

$$V_{BB} = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} = \frac{10k\Omega}{39k\Omega + 10k\Omega} \times 15V$$

$$= 3.06V$$

输入电阻

(电压源短路, 两端开路)

$$R_B = R_{B1} // R_{B2}$$

$$= 7.96k\Omega$$

由KVL:

$$V_{BB} = I_{BQ} R_B + U_{BEQ} + I_{EQ} R_E$$

且有

$$I_{EQ} = (1 + \beta) I_{BQ}$$

$$\therefore V_{BB} = I_{BQ} R_B + U_{BEQ} + (1 + \beta) I_{BQ} R_E$$

$$\therefore I_{BQ} = \frac{V_{BB} - U_{BEQ}}{R_B + (1 + \beta) R_E}$$

其中 $U_{BEQ} = 0.7V$

$$\therefore I_{BQ} = \frac{3.06V - 0.7V}{7.96k\Omega + 101 \times 1k\Omega} = 0.216mA$$

$$\therefore I_{CQ} = \beta I_{BQ} = 2.17mA$$



$$V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EQ} R_E$$

$$= V_{CC} - I_{CQ} (R_C + R_E)$$

$$= 15V - 2.17mA \times (2.7k\Omega + 1k\Omega)$$

$$= 15V - 6.971V$$

交流通路

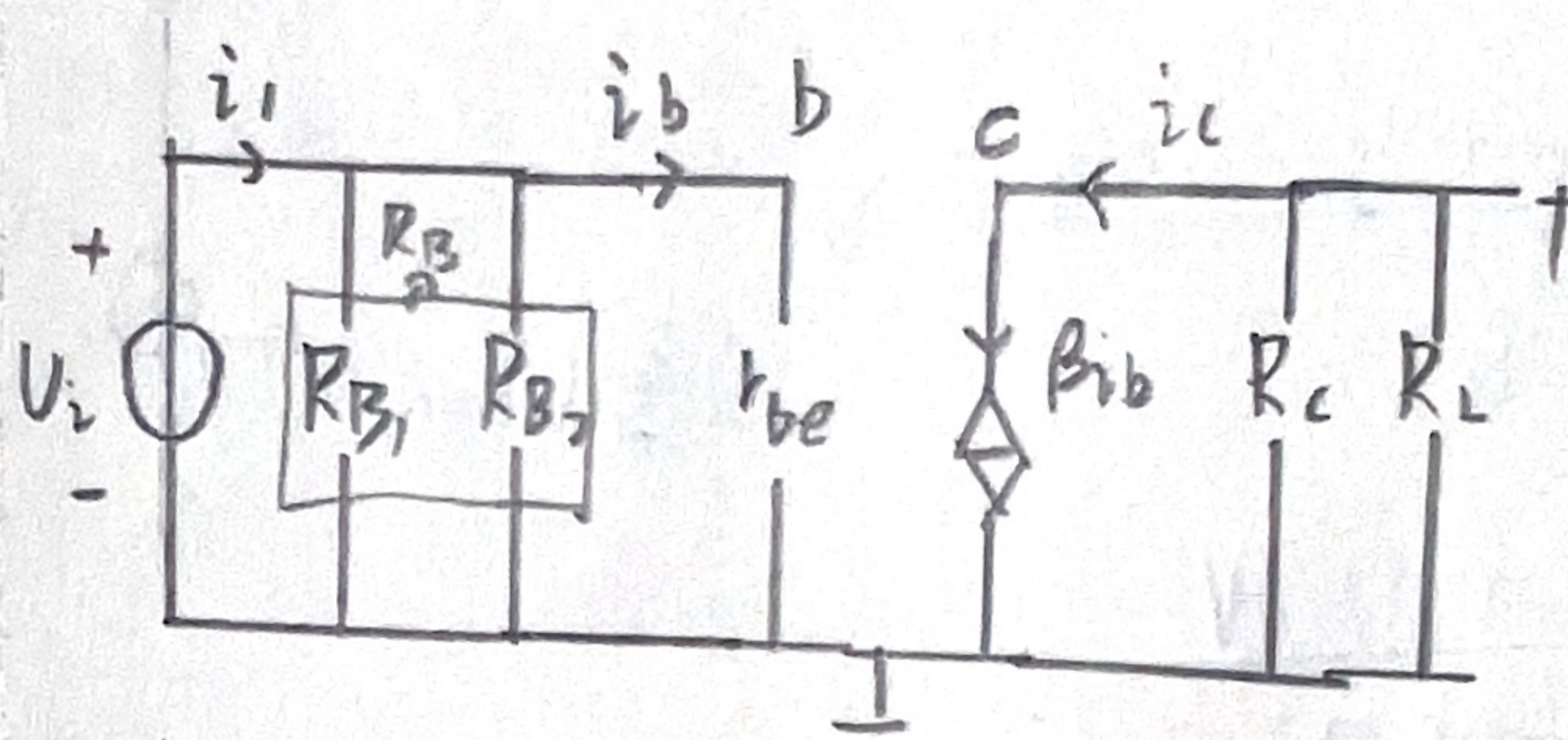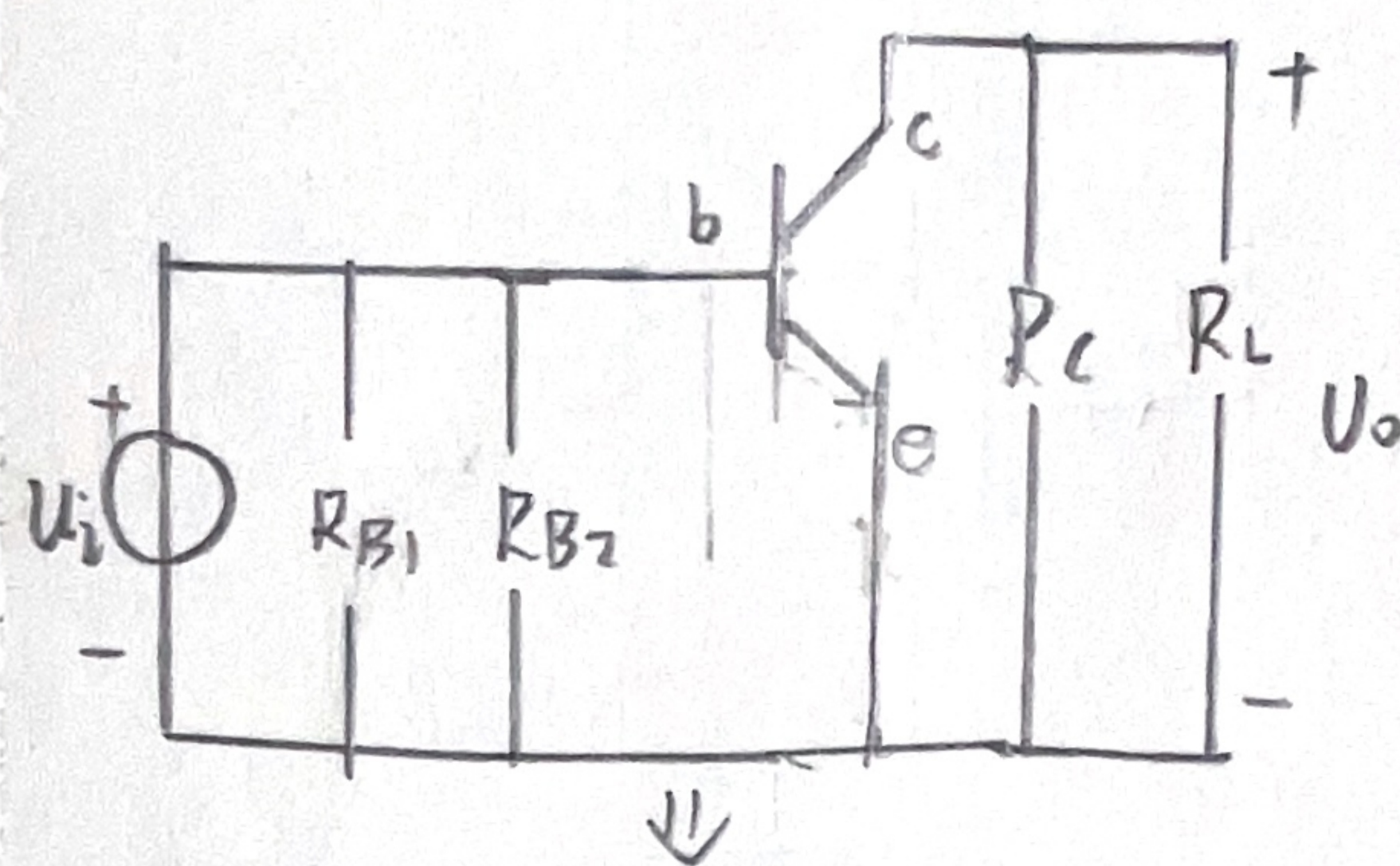

其中

$$r_{be} = r_{bb'} + (1 + \beta) r_e$$

$$= r_{bb'} + (1 + \beta) \frac{U_T}{I_{EQ}}$$

$$= r_{bb'} + (1 + \beta) \frac{26mV}{2.17mA + 0.216mA}$$

$$= 300\Omega + (1 + 100) \frac{26mV}{2.17mA + 0.216mA}$$

$$= 1.4k\Omega$$

$\dot{A}_u =$