

# 一、填空题

1. 图 4.3.1 所示电路中的电流  $i = \underline{\sqrt{2} \angle -45^\circ \text{ A}}$ 。

用电路等效简化电路


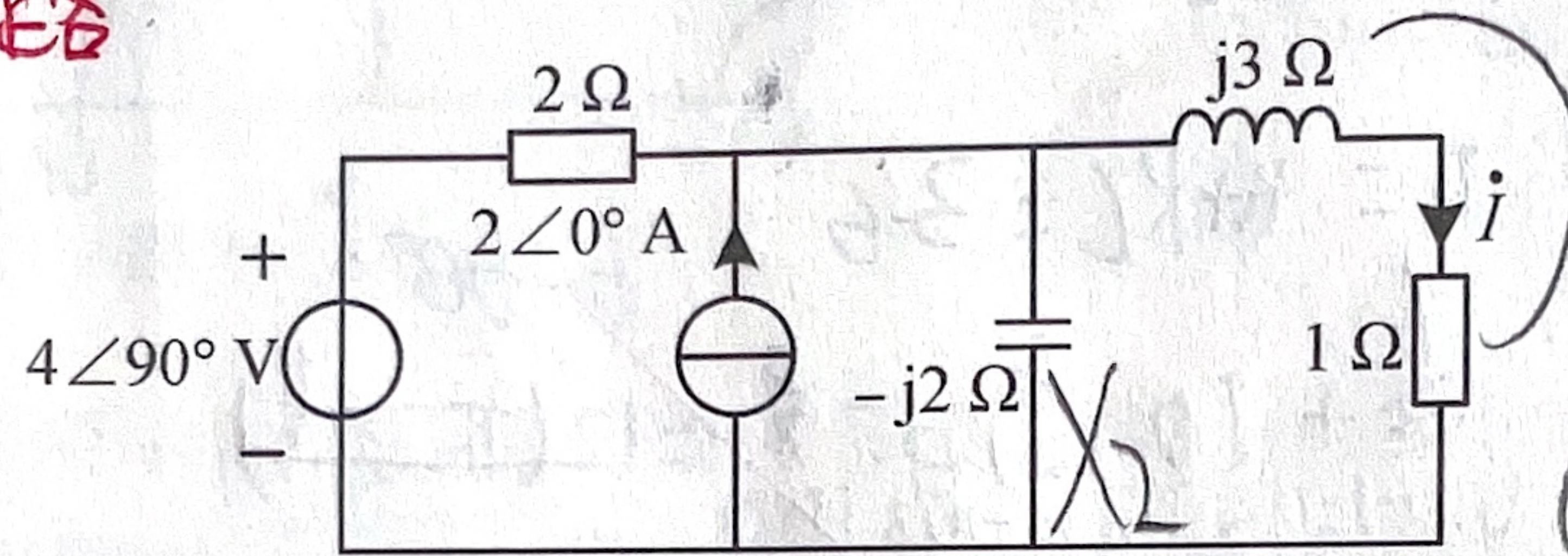
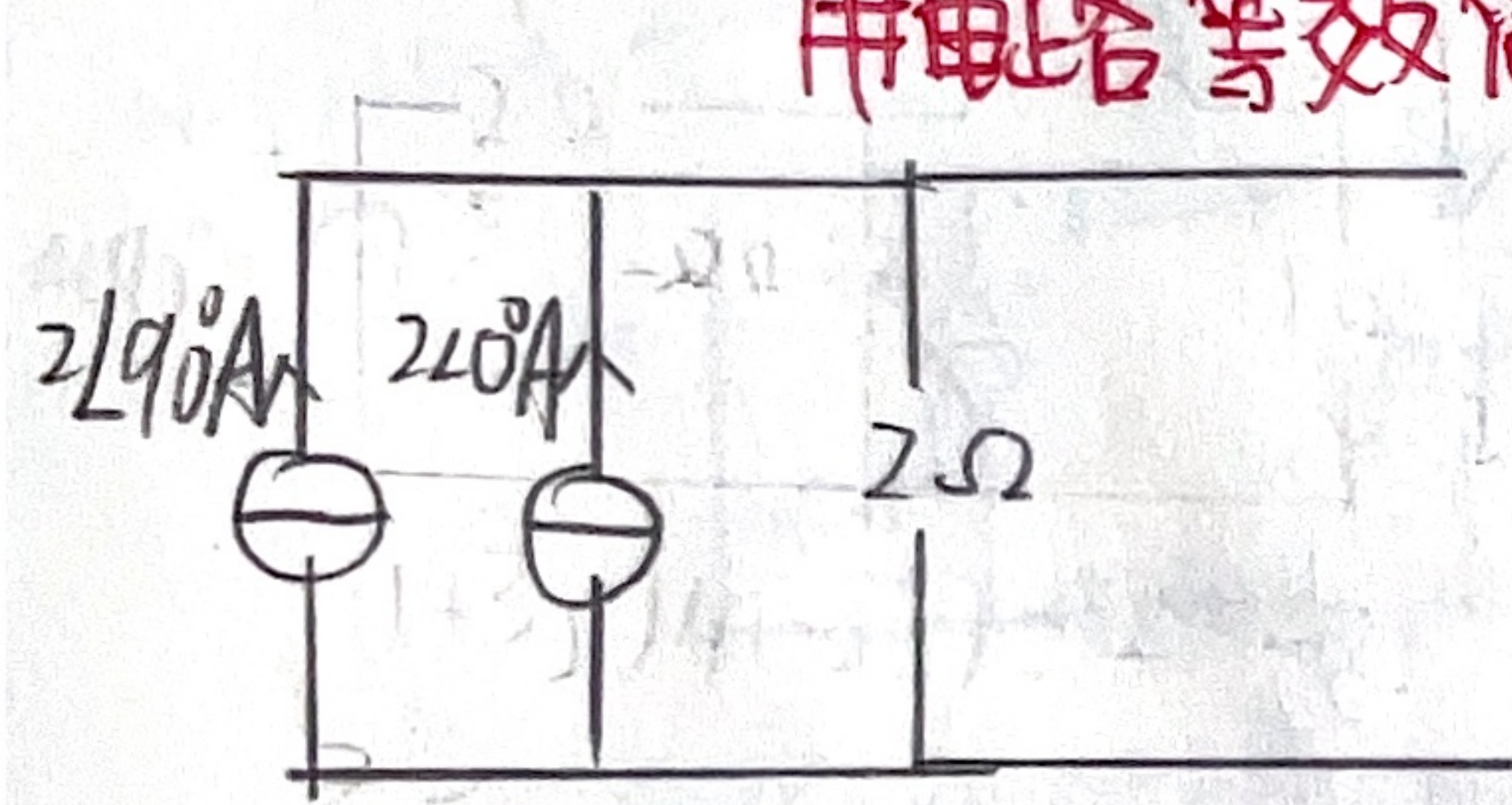


图 4.3.1

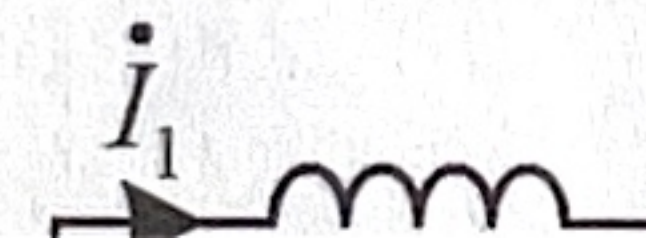
2. 图 4.3.2 所示电路中的电压  $\dot{U} = \underline{4j}$ 。

$$U - 2j \dot{I}_1 + 2(\dot{I}_1 + \dot{I}_3) = 0 \quad \text{--- ①}$$



$$2\angle 90^\circ + 2\angle 0^\circ = 2 + 2j = 2\sqrt{2} \angle 45^\circ$$

$$\cancel{(2j) // (1 + 3j) = 2 - 4j}$$

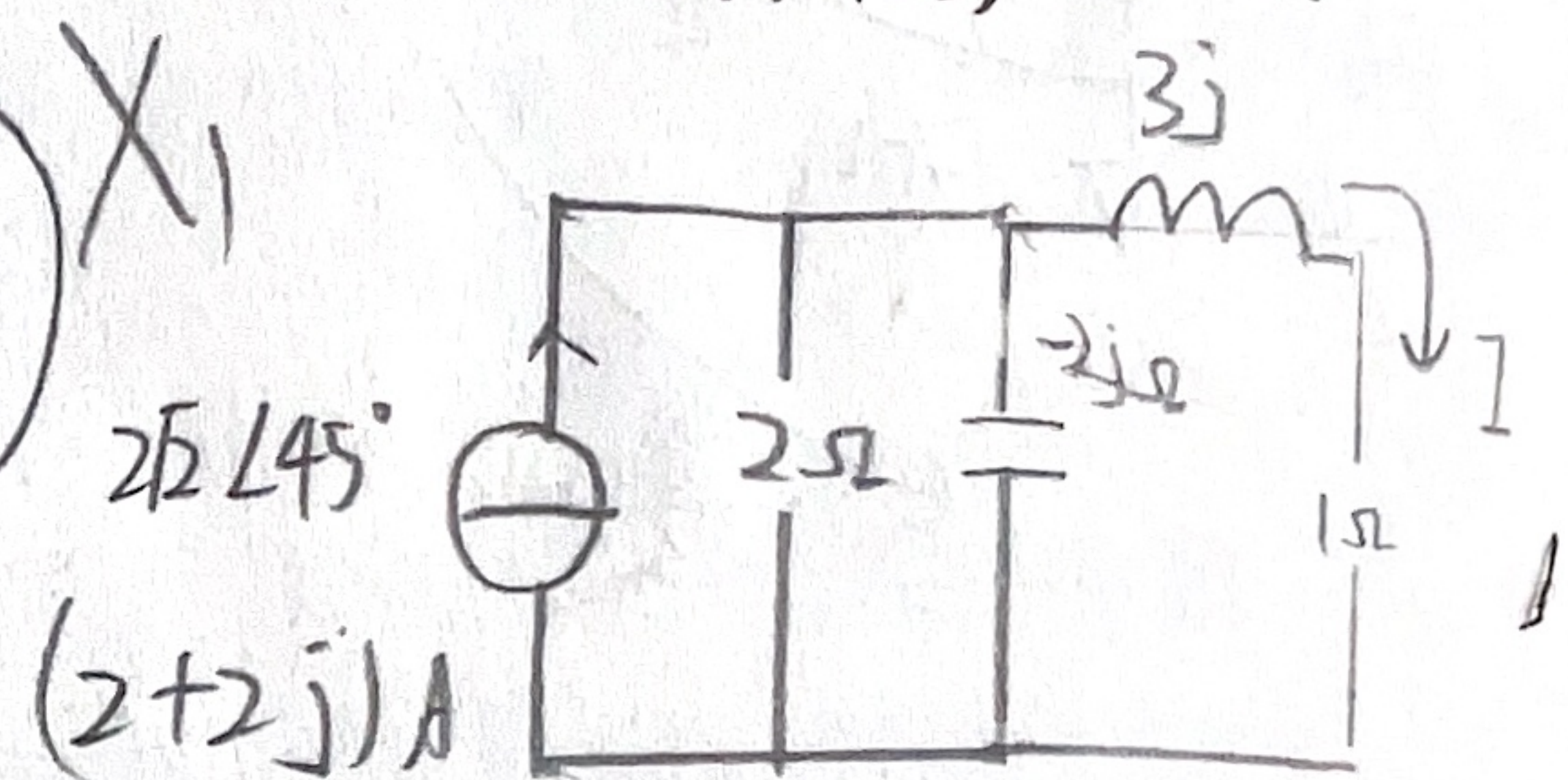

$$2 // -2j // (1 + 3j)$$

$$\frac{\frac{1}{1+3j}}{\frac{1}{1+3j} + \frac{1}{-2j} + \frac{1}{2}} \cdot (2+2j)$$