

$$i_c = C \cdot \frac{dv_c}{dt}, \quad i_2 = \frac{v_c}{4\Omega} = \frac{1}{4} v_c$$

$$i_c + i_2 = C \cdot \frac{dv_c}{dt} + \frac{1}{4} v_c \quad \text{--- (1)}$$

$$v_L = L \cdot \frac{di_L}{dt}$$

$$i_1 = \frac{v_L}{6\Omega} = \frac{1}{6} L \cdot \frac{di_L}{dt}$$

~~not in~~

$$i_L + i_1 = i_L + \frac{1}{6} L \cdot \frac{di_L}{dt} \quad \text{--- (2)}$$

$$\frac{1}{4} v_c + C \cdot \frac{dv_c}{dt} = 1$$

$$\frac{1}{4} v_c + \frac{1}{8} \cdot \frac{dv_c}{dt} = 1$$

$$\frac{1}{8} \cdot \frac{dv_c}{dt} = 1 - \frac{1}{4} v_c$$

$$\frac{dv_c}{dt} = 8 - 2v_c$$

$$= 2(4 - v_c)$$

~~8-2v_c~~

$$\frac{dv_c}{4 - v_c} = 2 dt$$

$$\frac{-d(4 - v_c)}{4 - v_c} = 2 dt$$

$$-\ln|4 - v_c| \Big|_0^t = 2t$$

$$\ln(v_c - 4) \Big|_0^t = -2t$$

$$\ln(v_c - 4) - \ln 6 = -2t$$

$$\ln(v_c - 4) = -2t + \ln 6$$

$$\ln(v_c - 4)$$

$$v_c - 4 = 6e^{-2t}$$

$$v_c = 6e^{-2t} + 4$$

$$i_L + \frac{1}{6} L \cdot \frac{di_L}{dt}$$

$$\ln(1 - i_L) \Big|_0^t = -3t$$

$$i_L + \frac{1}{3} \cdot \frac{di_L}{dt} = 1 \quad \ln(1 - i_L) = -3t$$

$$\frac{1}{3} \cdot \frac{di_L}{dt} = 1 - i_L \quad 1 - i_L = e^{-3t}$$

$$\frac{di_L}{1 - i_L} = 3 dt$$

$$i_L = 1 - e^{-3t}$$

$$\frac{d(1 - i_L)}{1 - i_L} = -3 dt$$

$$\frac{di_L}{dt} = 3e^{-3t}$$

$$\ln|1 - i_L| \Big|_0^t = -3t$$

$$L \cdot \frac{di_L}{dt} = 6e^{-3t}$$