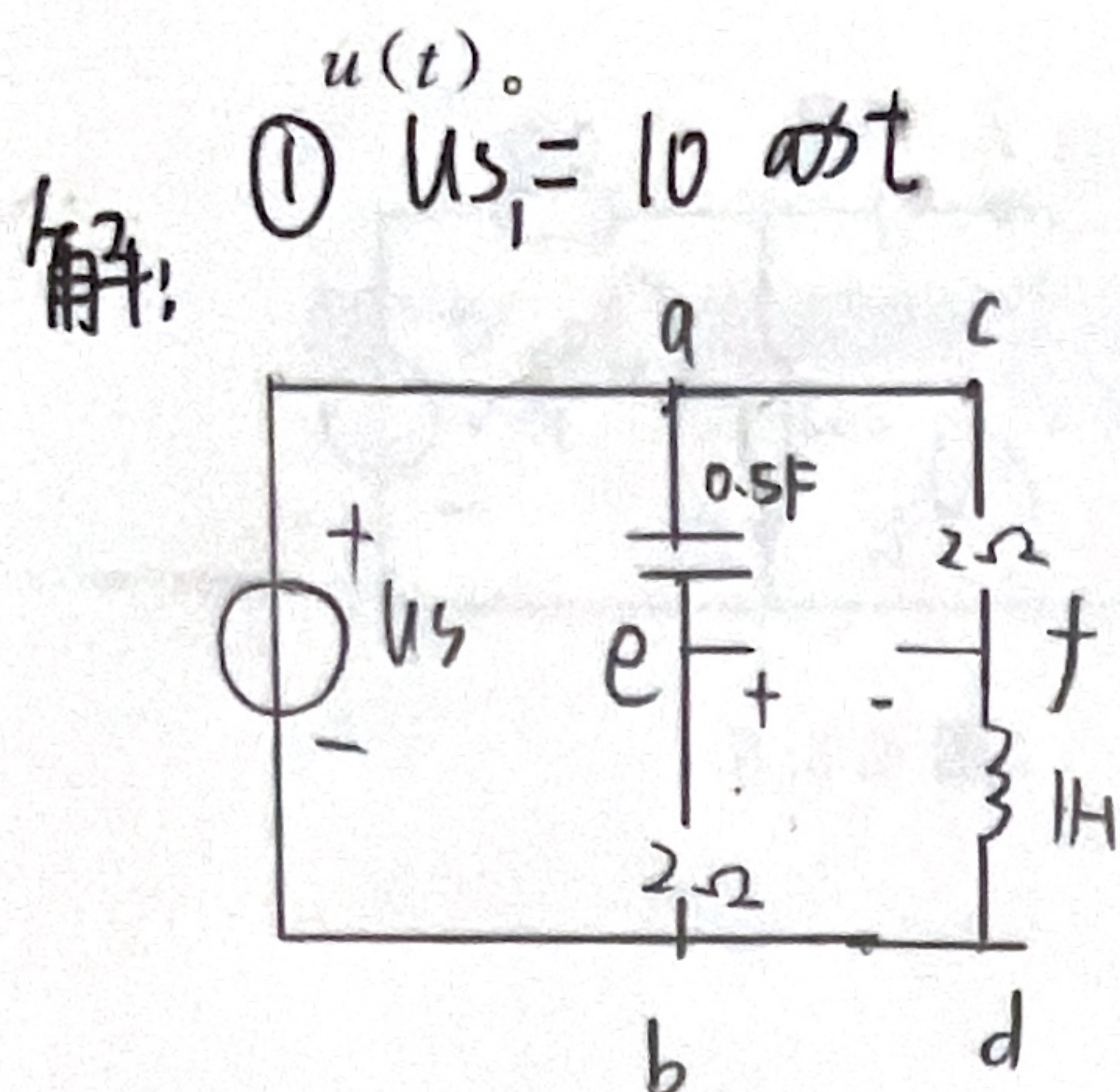


$$= 10 \angle 0^\circ$$

$$10 \cos t = 10 \cos t$$

$$5 \cos 2t$$

四、电路如图 4.3.7 所示, 已知 $u_s(t) = 10 + 10 \cos t$ (V), $i_s(t) = 5 + 5 \cos(2t)$ (A), 求



$$Z_{ab} = \frac{1}{j\omega C} \parallel R + \frac{1}{j\omega L}$$

$$= -j2 - \frac{1}{2j} = 2 - 2j$$

$$Z_{cd} = R + j\omega L$$

$$= 2 + j$$

$$U_{ab} = \frac{2}{2 + 2 - 2j} \cdot U_{s1}$$

$$= \frac{1}{1 - j} \cdot 10 \angle 0^\circ$$

$$= \frac{10}{1 - j}$$

$$= 5(1 + j) = 5 + 5j$$

② $U_{s2} = 10V$

$$U_{cd} = \frac{j}{2 + j} \cdot U_{s1}$$


$$= \frac{j}{2 + j} \cdot 10 \angle 0^\circ$$

$$= 2 + 4j$$

$$\therefore U_{ef} = U_{ab} - U_{cd} = (3 + j)(V)$$

$$\therefore U = (3 + j)(V)$$

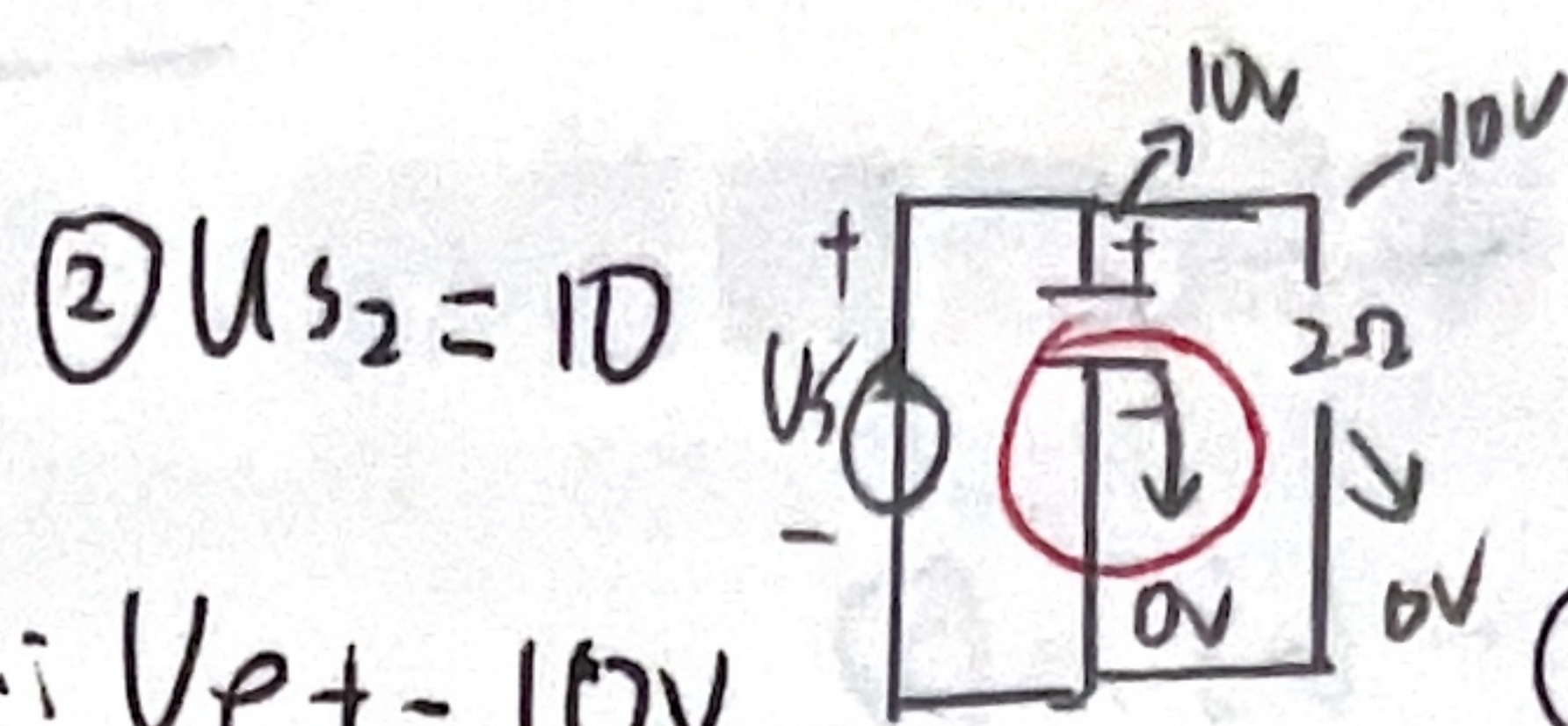
$$\therefore u(t) = \sqrt{10} \cos(t + 18.43^\circ) (V)$$



$$\therefore U_{ef} = 10V$$


$$\therefore U = 10V$$

③ $i_{s1}(t) = 5 \cos 2t$

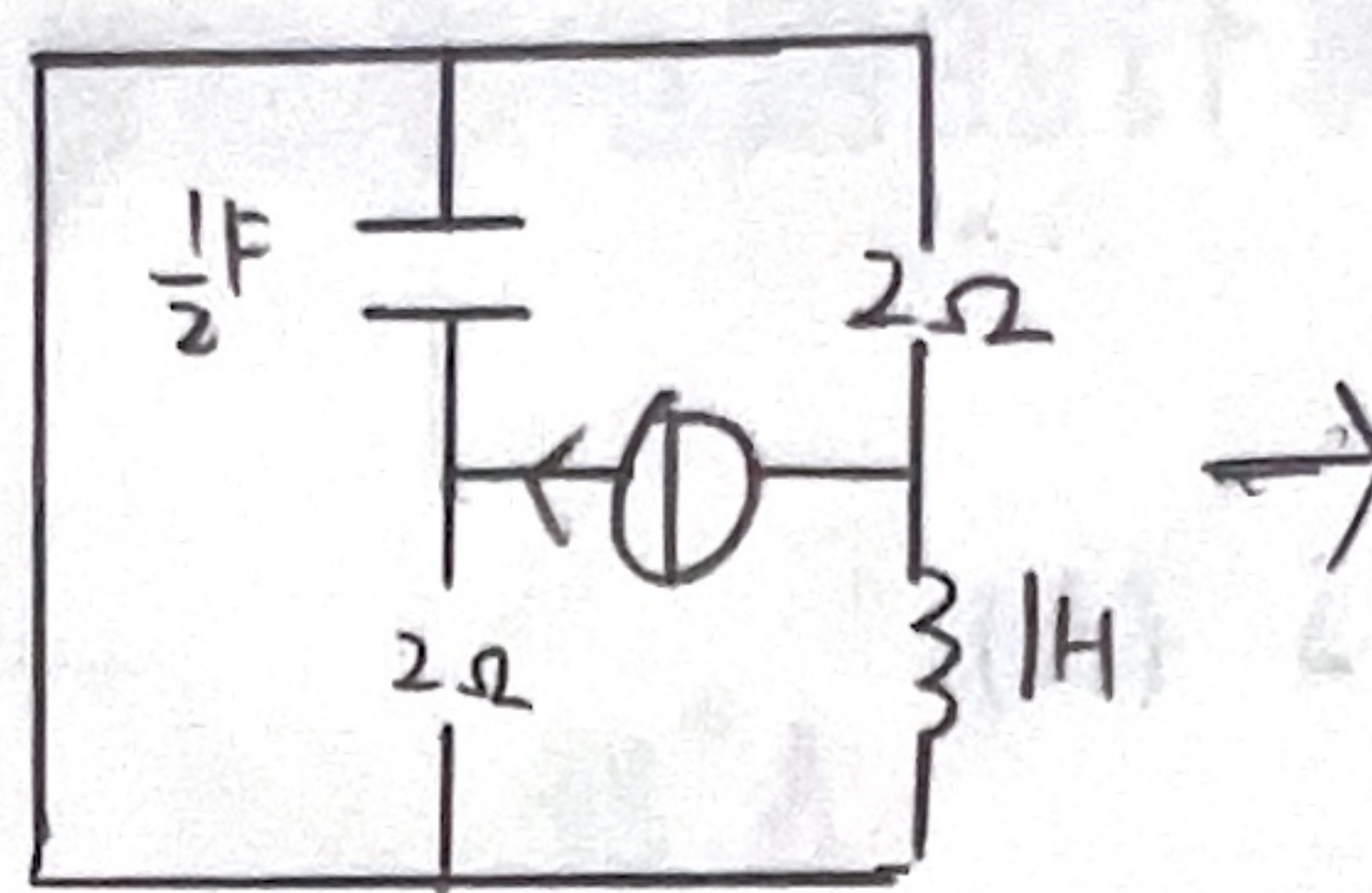

$$i_s = i_{s1}(t) = 5 \cos 2t$$

电路等效为

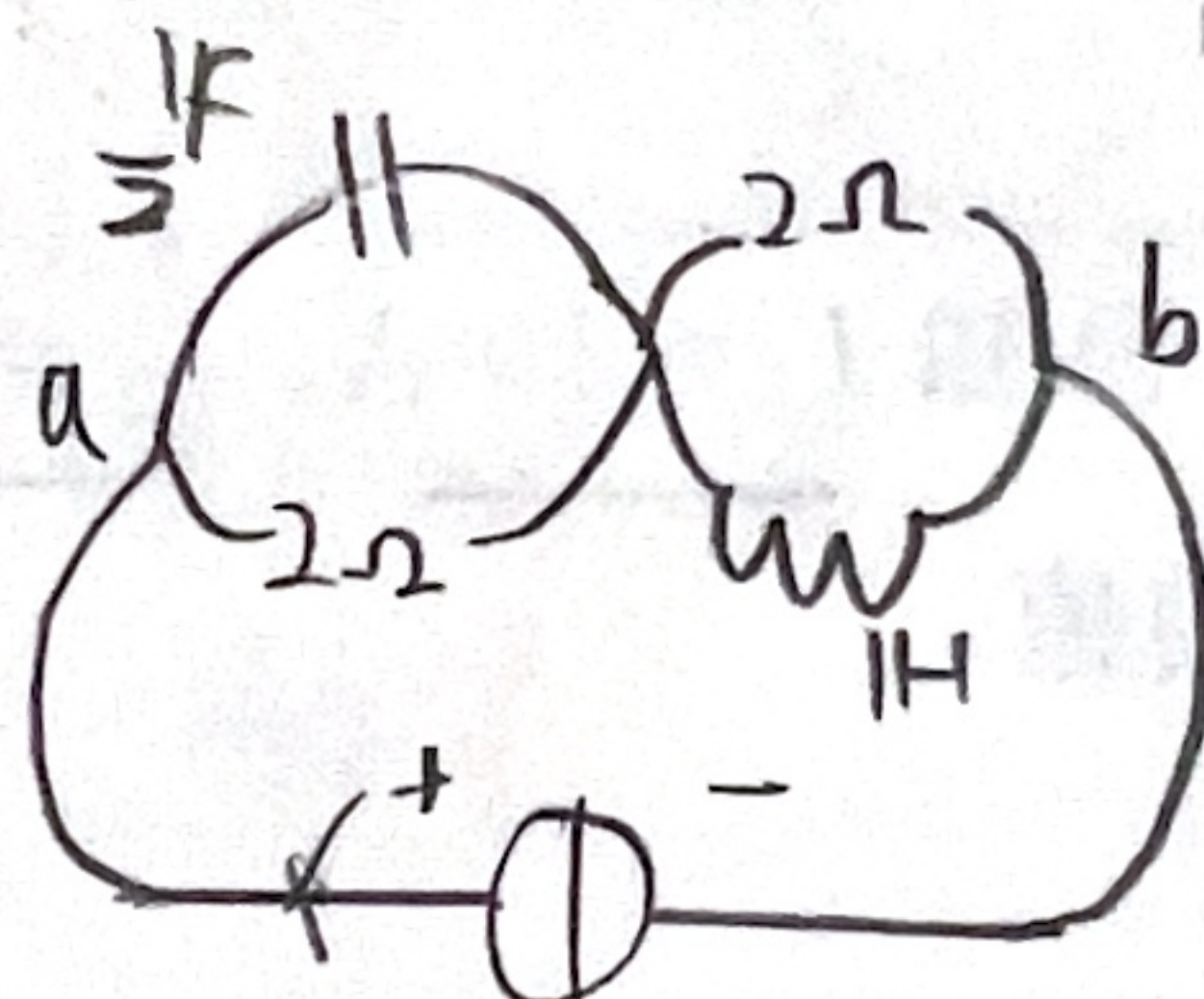

$$Z_{ab} = \left[\left(-j \frac{1}{\omega C} \parallel R \right) + (j\omega L \parallel R) \right]$$

$$= \left[\left(-j \parallel 2 \right) + (2j \parallel 2) \right]$$

$$= \frac{7}{5} + \frac{1}{5}j$$

$$\therefore U = Z_{ab} \cdot i_{s1}(t)$$

$$= \left(\frac{7}{5} + \frac{1}{5}j \right) 5$$

$$= 7 + j$$

$$\therefore u(t) = \sqrt{50} \cos(2t + 8.31^\circ) (V)$$

④ $i_{s2}(t) = 5A$

$$U = 10V$$

$$\therefore u(t) = 10 + \sqrt{10} \cos$$

$$\therefore u(t) = 10 + \sqrt{10} \cos$$

$$\therefore u(t) = \sqrt{10} \cos(t + 18.43^\circ) + \sqrt{50} \cos(2t + 8.31^\circ) + 10 V$$

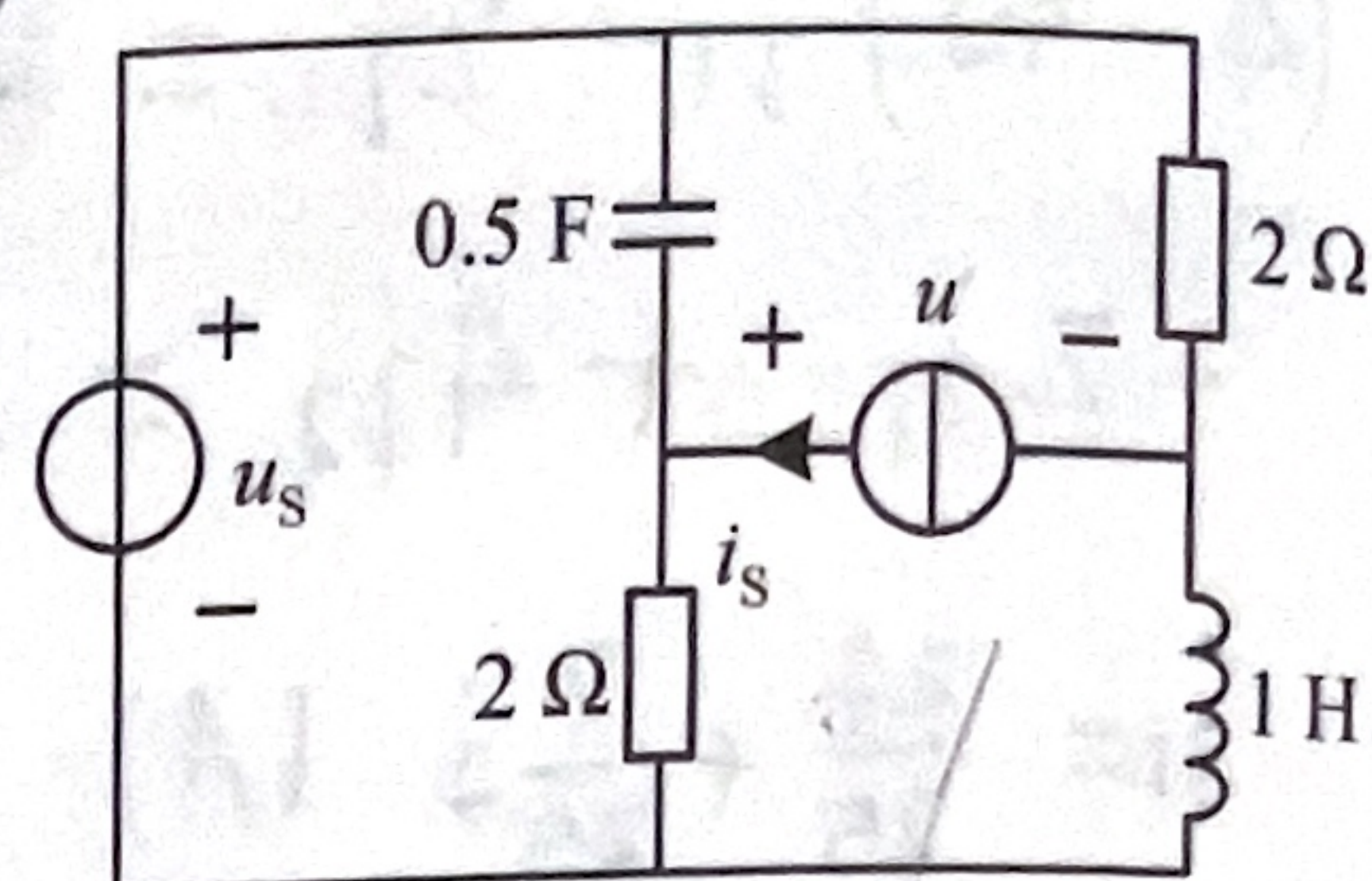


图 4.3.7

