

5. 电路如图 2.5.5 所示, 则其 a、b 端的戴维南等效电路中的 $u_{OC} = \underline{4V}$, $R_0 = \underline{1\Omega}$ 。
 外加电源法 短路法 外加电源法

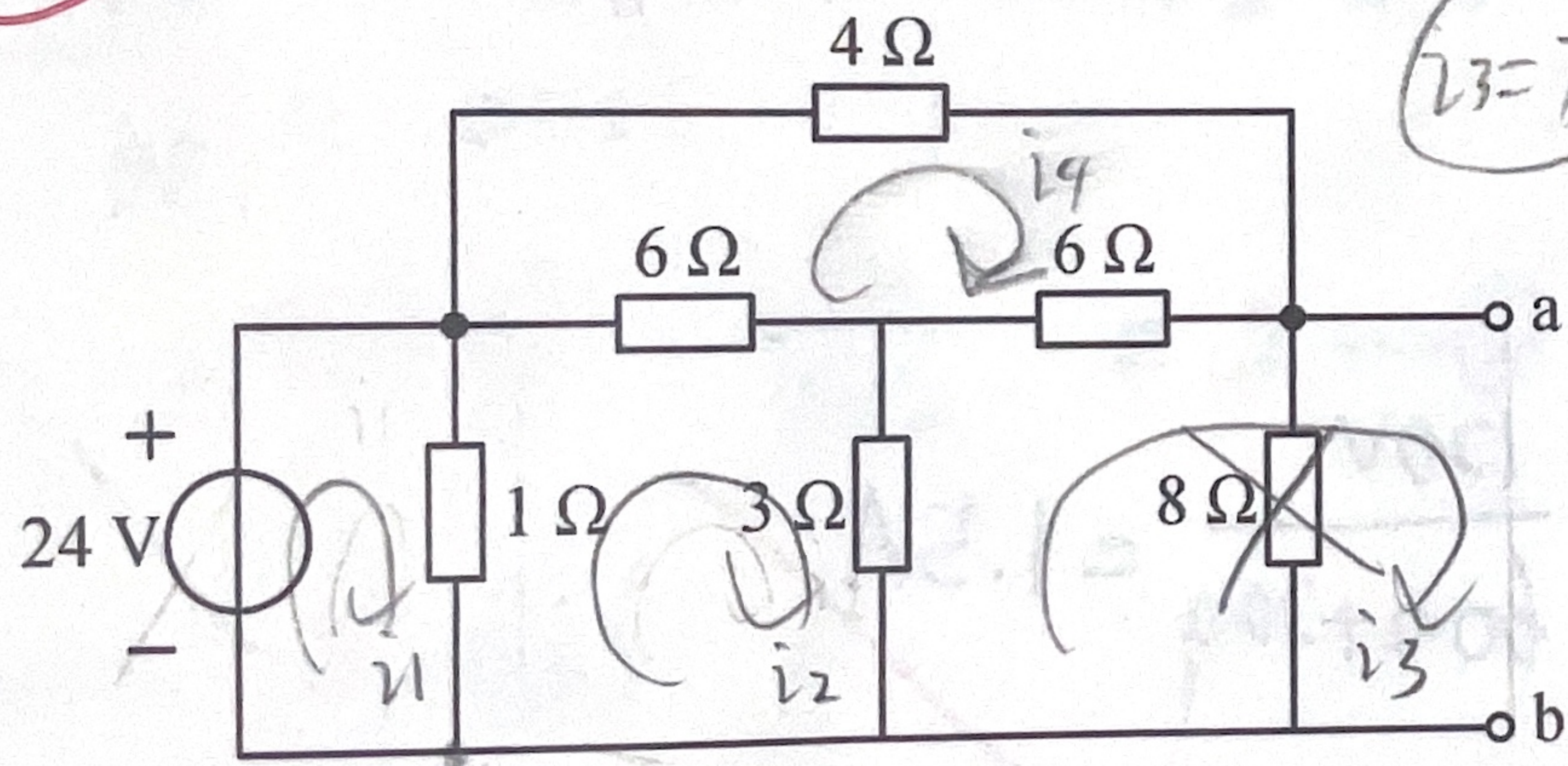


图 2.5.4


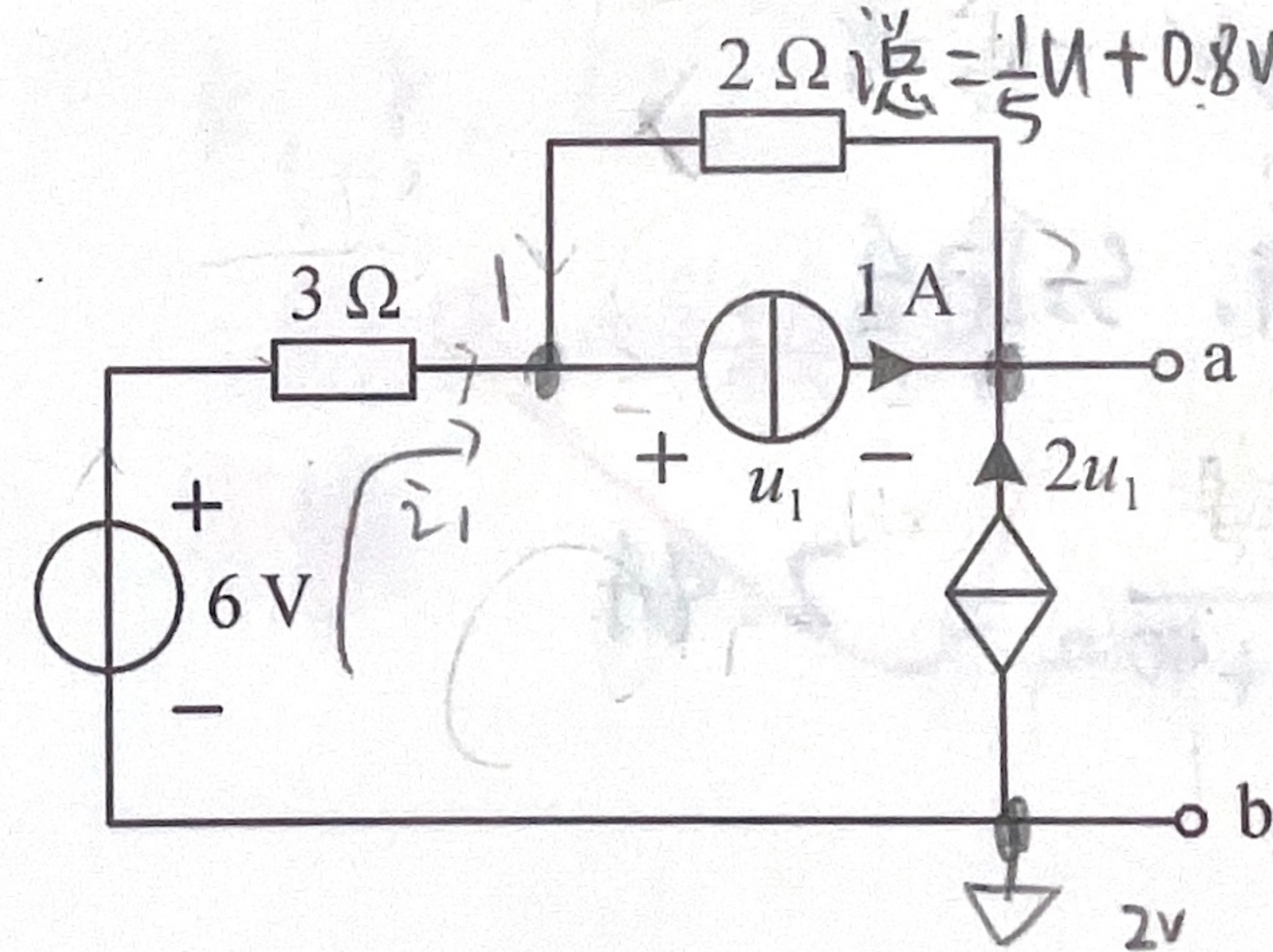
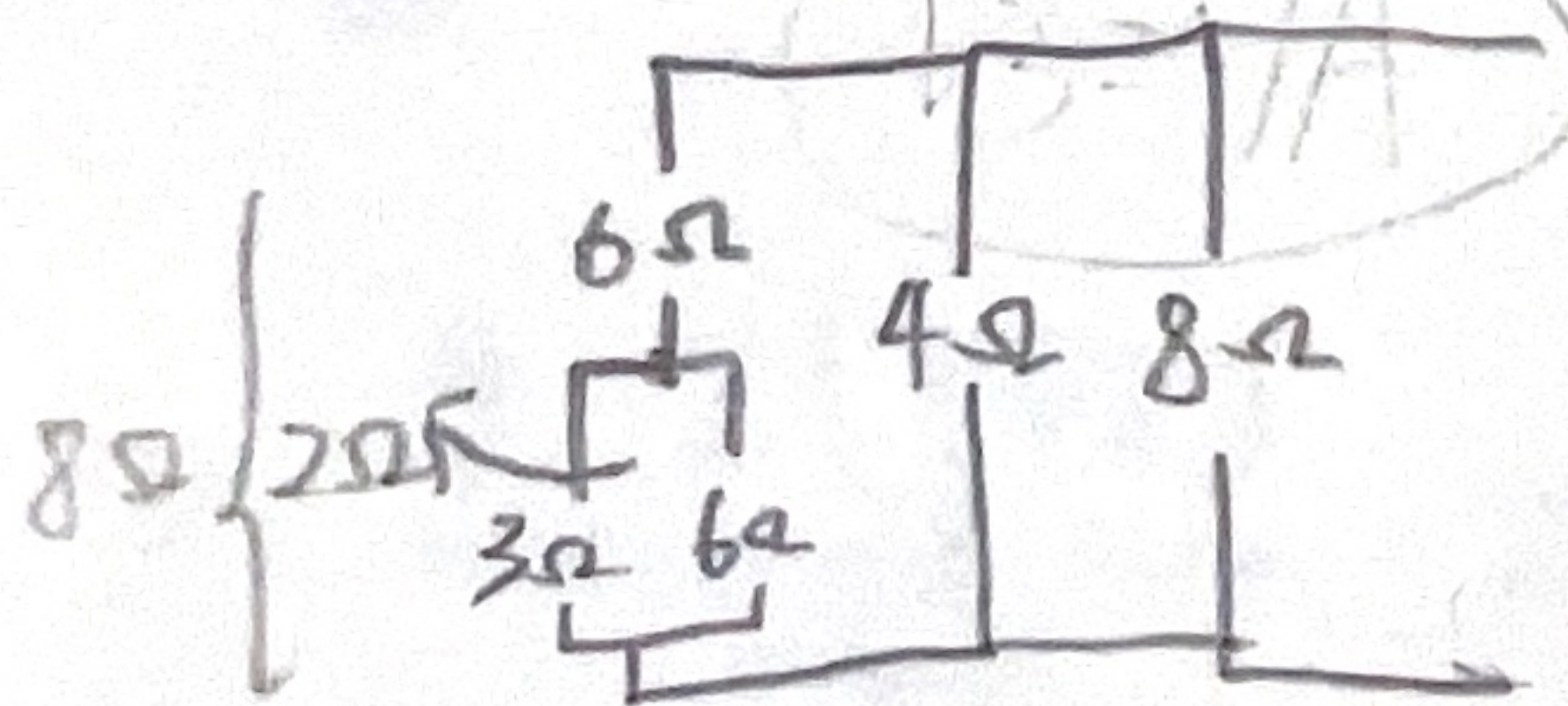


图 2.5.5

$$\begin{cases} (\frac{1}{3} + \frac{1}{2})\varphi_1 - \frac{1}{2}\varphi_2 = 2 - 1 - \text{①} \\ -\frac{1}{2}\varphi_1 + \frac{1}{2}\varphi_2 = 1 + 2(\varphi_1 - \varphi_2) - \text{②} \end{cases}$$
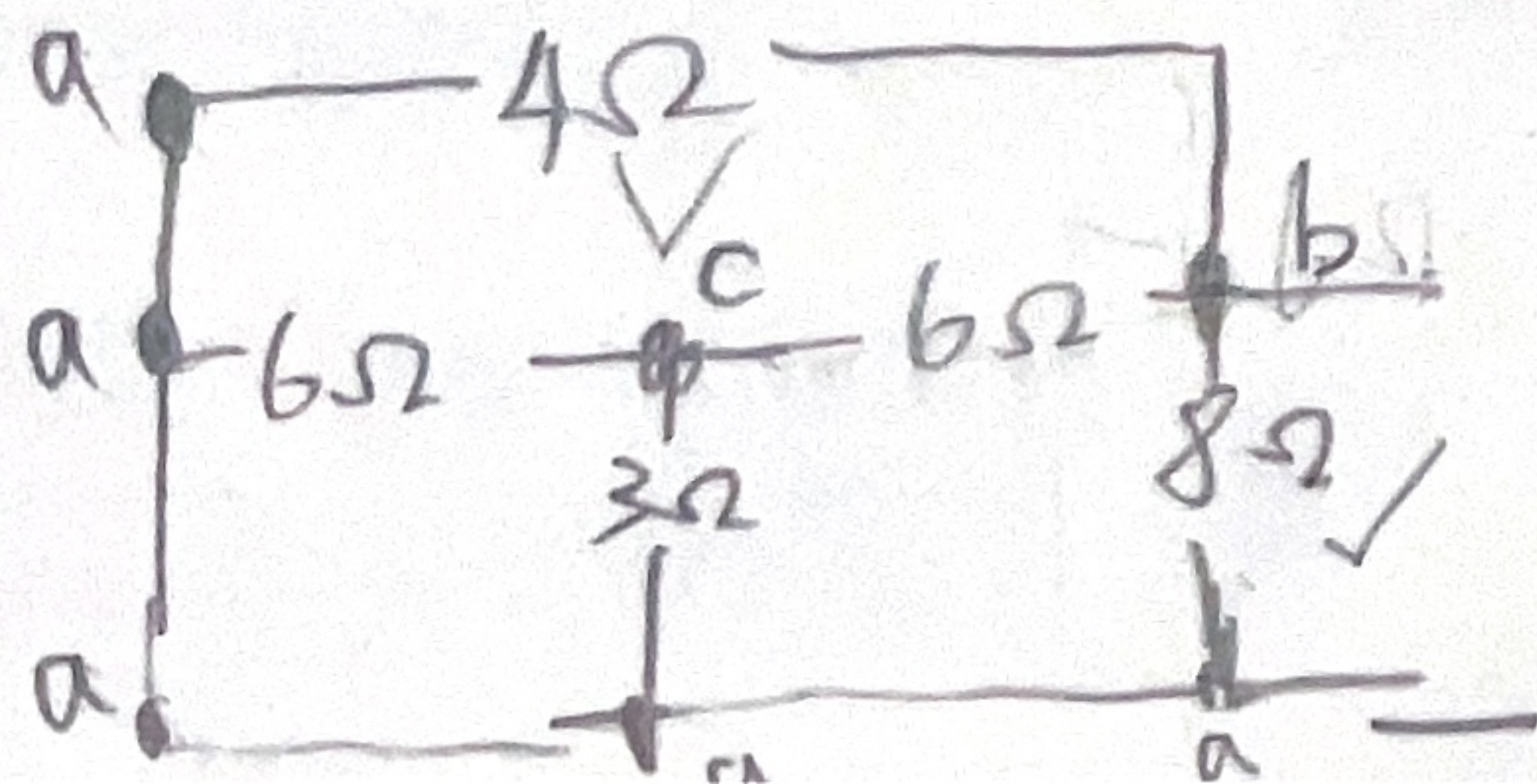
$$\Rightarrow \varphi_1 = \frac{18}{5}, \varphi_2 = 4, u_{OC} = \varphi_2 = 4V$$

